



NATIONAL OPEN UNIVERSITY OF NIGERIA
14-16 AHMADU BELLO WAY, VICTORIA ISLAND, LAGOS
SCHOOL OF SCIENCE AND TECHNOLOGY
JANUARY/FEBRUARY 2013 EXAMINATION

COURSE CODE: PHY 308

COURSE TITLE: ELECTRONICS I

CREDIT UNIT: 3

INSTRUCTION: Answer any five questions.


TIME: 3 Hours

1. (a) (i) What is an amplifier? List the main properties of an amplifier and draw a simple circuit diagram of an ideal amplifier to show the relationship among these properties. 5 marks

(ii) Determine the Voltage, Current and Power Gain of an amplifier that has an input signal of 1mA at 10mV and a corresponding output signal of 10mA at 1V . Also, express all three gains in decibels, (dB). 5 marks

(b) (i) Distinguish between the A and B classes of amplifier. With sketch transfer characteristic curves, show the relationship between the input and the output signals of each class. State an advantage of one class over the other. 5 marks

(ii)

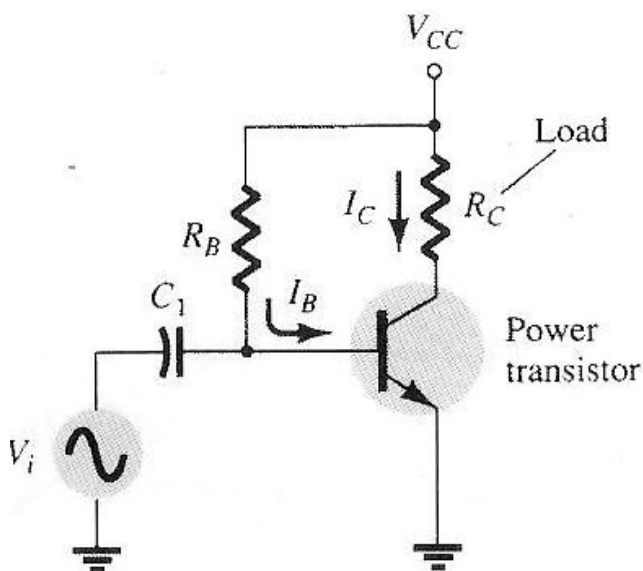

Series-fed class A large signal amplifier

The figure shown is a circuit diagram for a series-fed class A large signal amplifier.

Given $R_B=1k\Omega$, $R_C=20\Omega$ $V_{CC}=20V$ and $\beta=25$, calculate V_{CE} .

5 marks

13020710
18


2. (a) (i) A transistor is a three-terminal device. With suitable diagrams, explain briefly the three main transistor configurations (connection in a practical circuit) for an NPN transistor. 6 marks

(ii) Show that the current amplification factors α and β are related by the equation

$$\beta = \frac{\alpha}{1-\alpha} \text{ where the symbols have the usual meaning}$$

4 marks

(b)

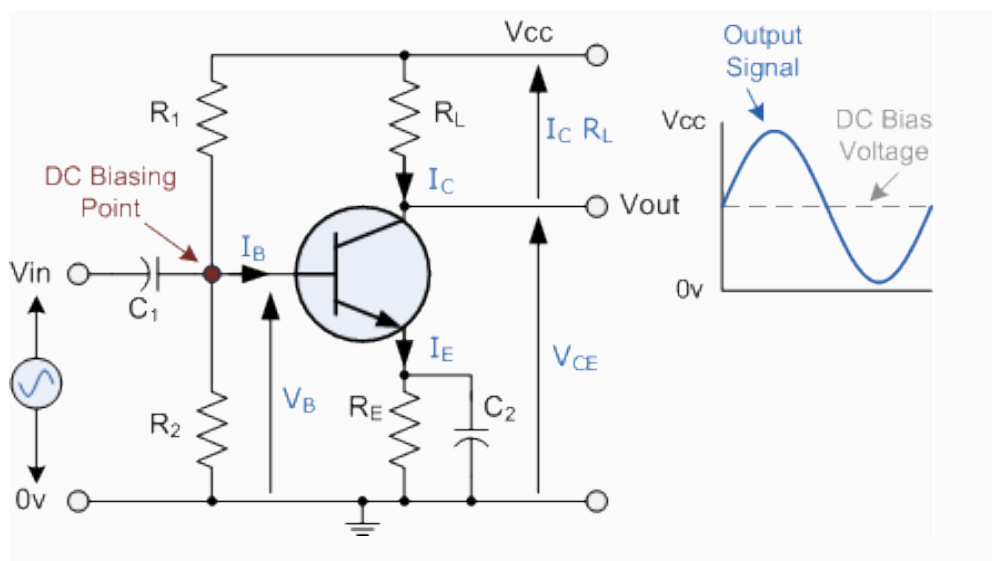

Circuit diagram for question 2 b

For the emitter bias circuit shown, calculate the values of R_1 , R_2 and R_E to provide a quiescent operating point of $I_C=1mA$ $V_{CE}=10V$. The transistor used in the circuit is silicon with a d.c. current gain at 1 mA of $h_{FE}=50$. Assume the base-emitter voltage $V_{BE}=0.7V$. The load resistor and collector supply voltage for the circuit are

$R_L=5k\Omega$, $V_{CC}=15V$

10 marks

3. (a) Given $I_E= 2.5 mA$, $h_{fe} = 140$, $h_{oc} = 20 \mu S$ (μmho) and $h_{ob} = 0.5 \mu S$, determine:

(i) The common-emitter hybrid equivalent circuit.

5 marks


(ii) The common-base r_e model

5 marks

13020710
18

(b)

1

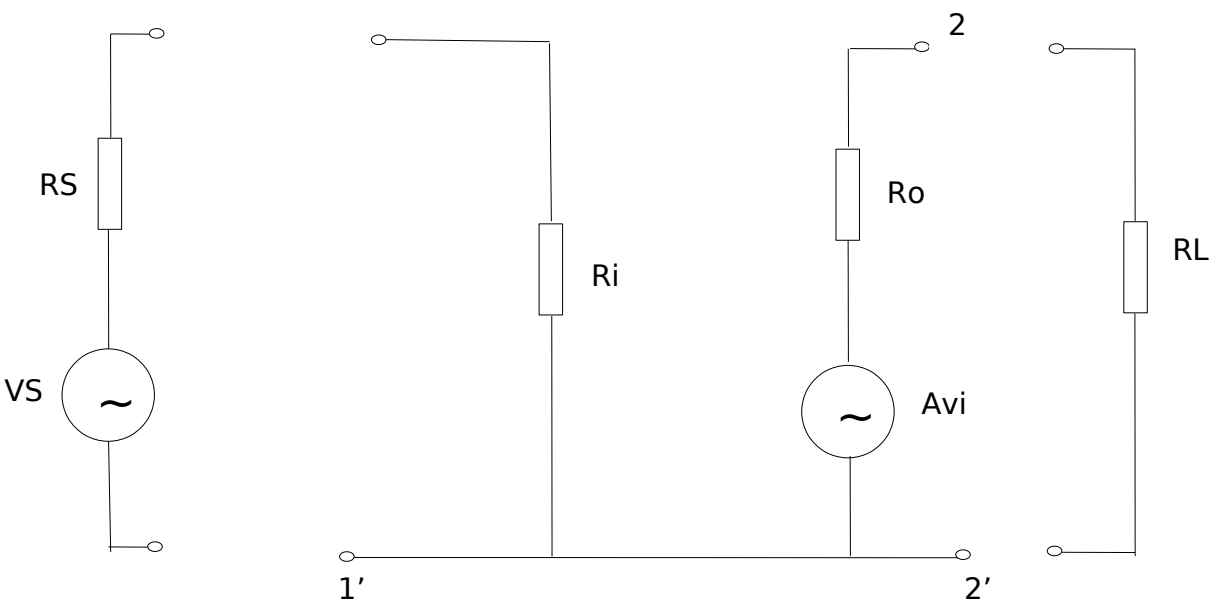

Circuit diagram for questions 3b

The figure shows an a.c. equivalent circuit of an amplifier. The input and output of the amplifier have values $R_i = 5\text{ k}\Omega$, $R_o = 50\text{ k}\Omega$. The open-circuit voltage amplification of the amplifier, $A = 250$. If the signal generator of peak amplitude $V_s = 10\text{ mV}$ and internal resistance $R_s = 600\Omega$ is connected across the input terminals 1-1' and a load resistance $R_L = 10\text{ k}\Omega$ is connected across the output terminals 2-2', use the equivalent circuit to determine:

- (i) peak value of the signal voltage across 1-1',
5 marks
- (ii) the peak values of the signal output current and signal voltage
5 marks

4 (a) (i) Complete the following table of h-parameter

Parameter	Meaning	Relation	Condition	Unit
h_{11}			Output shorted	Ohm
	Reverse voltage gain	$\frac{V_i}{V_o}$		dimensionless
h_{21}	Current gain	$\frac{I_o}{I_i}$		

h_{22}	$\frac{I_o}{V_o}$	Input open
----------	-------------------	------------

4 marks

(ii) List four factors on which the h-parameter depend

2 marks

(b) Given $I_E = 2.5 \text{ mA}$, $h_{fe} = 140$, $h_{oc} = 20 \mu\text{S}$ (μmho) and $h_{ob} = 0.5 \mu\text{S}$, determine

13020710
18

(i) The common-emitter hybrid equivalent circuit
marks

8

(ii) The common-base r_e model

6 marks


5 (a) (i) Briefly explain the term *operating point*

3 marks

(ii) Summarize the operation in the cutoff, saturation, and linear regions of the BJT characteristic.

5 marks

(b)

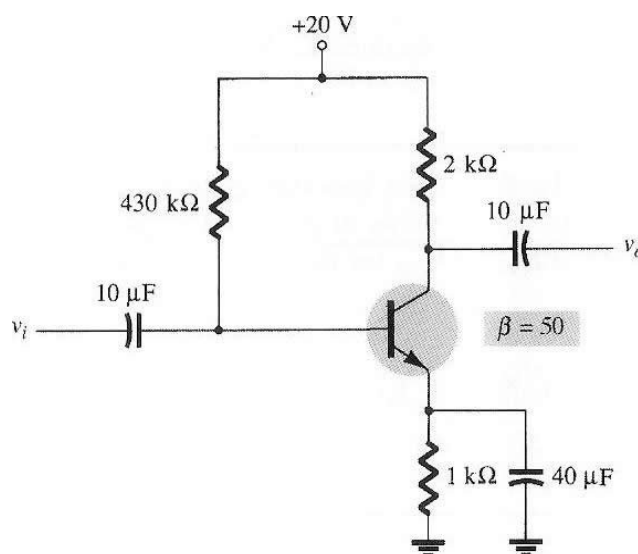

For the emitter bias network shown determine: I_B , I_C , V_{CE} , V_C , V_E , V_B , V_{BC} .
marks

12

6(a) (i) What is an *oscillator*?

2 marks

(ii) Briefly, distinguish between positive and negative feedback as applied to an oscillator. 6 marks

(b) (i) Draw the circuit diagram for closed-loop non-inverting operational amplifier. 4 marks (ii) For the closed-loop non-inverting operational amplifier, show that

$A' = \frac{R_i + R_f}{R_i}$, where the A' is the voltage gain. $R_i \wedge R_f$ are the resistances in the input and feedback paths respectively. 8 marks

7 (a) (i) Explain the usefulness of a rectifier circuit in a dc supply unit 2marks

(ii) Draw the circuit diagram of the half-wave rectifier circuit and indicate the respective input and output waveforms

7 marks (b) (i) A half-wave rectifier using silicon diode has a secondary *emf* of 14.14 V (rms) with a resistance of $0.2\ \Omega$. The diode has a forward resistance of $0.05\ \Omega$ and a threshold voltage of 0.7 V . If load resistance is $10\ \Omega$, determine: dc load current, dc load voltage, voltage regulation and efficiency.

6 marks

(ii) Draw the diagram of the full-wave rectifier circuit using the centre-tapped transformer and briefly explain how it works.

5 marks

13020710
18