



**NATIONAL OPEN UNIVERSITY OF NIGERIA
14-16 AHMADU BELLO WAY, VICTORIA ISLAND LAGOS
SCHOOL OF SCIENCE AND TECHNOLOGY
MARCH/APRIL 2015 EXAMINATION**

SCHOOL OF SCIENCE AND TECHNOLOGY


COURSE CODE: PHY 405
COURSE TITLE: Electronics III
TIME: 3 Hours

INSTRUCTION: Answer question 1 and any other four questions.

1. (a) (i) Draw a circuit diagram to show how the **OR** gate can be realized using two pn junction diodes.

3 marks

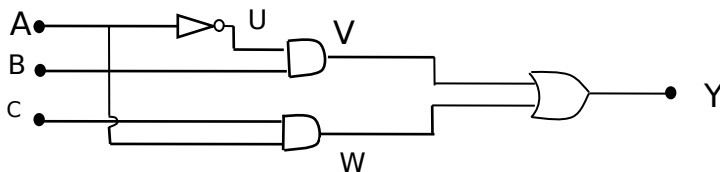(ii) Draw the circuit symbol of the **NOR** gate and construct its truth-table **4 marks**



Use this circuit diagram for Q2

(b) Use the circuit diagram shown to answer the following questions:

(i) Write down the outputs U, V, W and Y in terms of the inputs A and B.

5 marks

(ii) Construct the truth-table of the output Y in terms of the input A and B.

2 marks

2. (a) (i) Convert the following to decimal number:

$3BE.1A_{16}$; $(1011.101)_2$

3 marks

(ii) Multiply 101101 by 110

3 marks

(b) Use Boolean theorems to prove the following identities:

(i) $A + \bar{A}B = A + B$

4 marks

(ii) $(A+B)(A+C) = A + BC$

4 marks

3(a) (i) Draw a half-adder circuit and label its inputs and outputs.

4marks

(ii) Construct the truth table to illustrate the operation of the half-adder circuit

4 marks

(b)(i) Draw a digital circuit diagram of a two-bit binary adder.

3 marks

(ii) Mention two examples of universal gates and briefly state the reason why they are referred to as universal.

3 marks

4. (a) (i) Distinguish between combinational and sequential logic circuits and give one example of each.

3 marks

(ii) With a suitable circuit diagram, explain the working of a RS flip-flop constructed with two NAND gates.

4 marks

(b) (i) Draw the circuit diagram of the De Morgan equivalent of the NAND gate RS flip-flop.

3 marks

(ii) Construct the truth table for a positive edge triggered RS flip-flop

4 marks

5. (a) (i) Write the Boolean expression for the truth table given in Table Q5.1 **4 marks**

Table Q5.1:

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(ii) Design a digital circuit for $Y = \bar{A}C + A\bar{D}$ using AND, OR and NOT gates. **4 marks**

(b) (i) Design a digital circuit for question 5(a)(ii) using NAND gates only **4 marks**

(ii) Distinguish between positive going transition PGT and negative going transition NGT as applied to edge triggered systems **2 marks**

6. (a) (i) What is a register?

2 marks

(ii) Draw a circuit diagram of a buffer register and explain its working.

5 marks

(b) (i) What is a counter? What do you understand by the mod number of a counter?

3 marks

(ii) Design a mod 12 counter.

4 marks

7. (a) (i) Draw a pictorial representation of a general purpose CRT and label the components.

4 marks

(ii) If the time/div control is set to $2 \mu\text{s/div}$ and the displayed signal covers 4 div on the horizontal scale of the CRT screen, determine the frequency of the signal. **4 marks**

(b) (i) What is a function generator?

3 marks

(ii) Distinguish between the terms rise time T_r and fall time T_f as applied to signal generation.

3 marks